

# Laboratory 5: Simple Processor

Bryan Guner and Haley Scott

ELC 363 – L2


December 4<sup>th</sup> 2016

## Introduction:

The purpose of this laboratory was to implement the architecture of a simple processor using Xilinx' design package for FPGAs and CPLDs. In order to accomplish said goal, considered a simple accumulator based processor, with a 16-bit word length.
 
## Problem Description:

In this experiment, students will be asked to implement the architecture of a simple processor. Students will study the controller flow diagram, as well as the Von Neuman approach. The architecture must utilize machine language to test the program, and use a clock period of 1 microsecond as the timing constraint. The students must follow the guidelines shown below.



If AM = 0, the addressing mode is direct, and if AM = 1, the addressing mode is indirect.

The machine has the following registers only.

| REGISTER NAME | FUNCTION                   | LENGTH  |
|---------------|----------------------------|---------|
| IR            | INSTRUCTION REGISTER       | 16 bits |
| MD            | MEMORY DATA REGISTER       | 16 bits |
| AC            | ACCUMULATOR                | 16 bits |
| PC            | PROGRAM COUNTER            | 12 bits |
| MA            | MEMORY ADDRESS<br>REGISTER | 12 bits |


The processor implements the following instructions only.

| OP CODE | MNEMONIC | DESCRIPTION    |
|---------|----------|----------------|
| 000     | NOT      | INVERT         |
| 001     | ADC      | ADD WITH CARRY |


| OP CODE | MNEMONIC | DESCRIPTION         |
|---------|----------|---------------------|
| 010     | JPA      | JUMP IF ACC > 0     |
| 011     | INCA     | INCREMENT ACC       |
| 100     | STA      | STORE AND CLEAR ACC |
| 101     | LDA      | LOAD ACCUMULATOR    |

Using the above constraints, students must utilize the controller flow diagram shown below. A block diagram of the assigned simple processor architecture is also shown below.

Controller flow diagram:

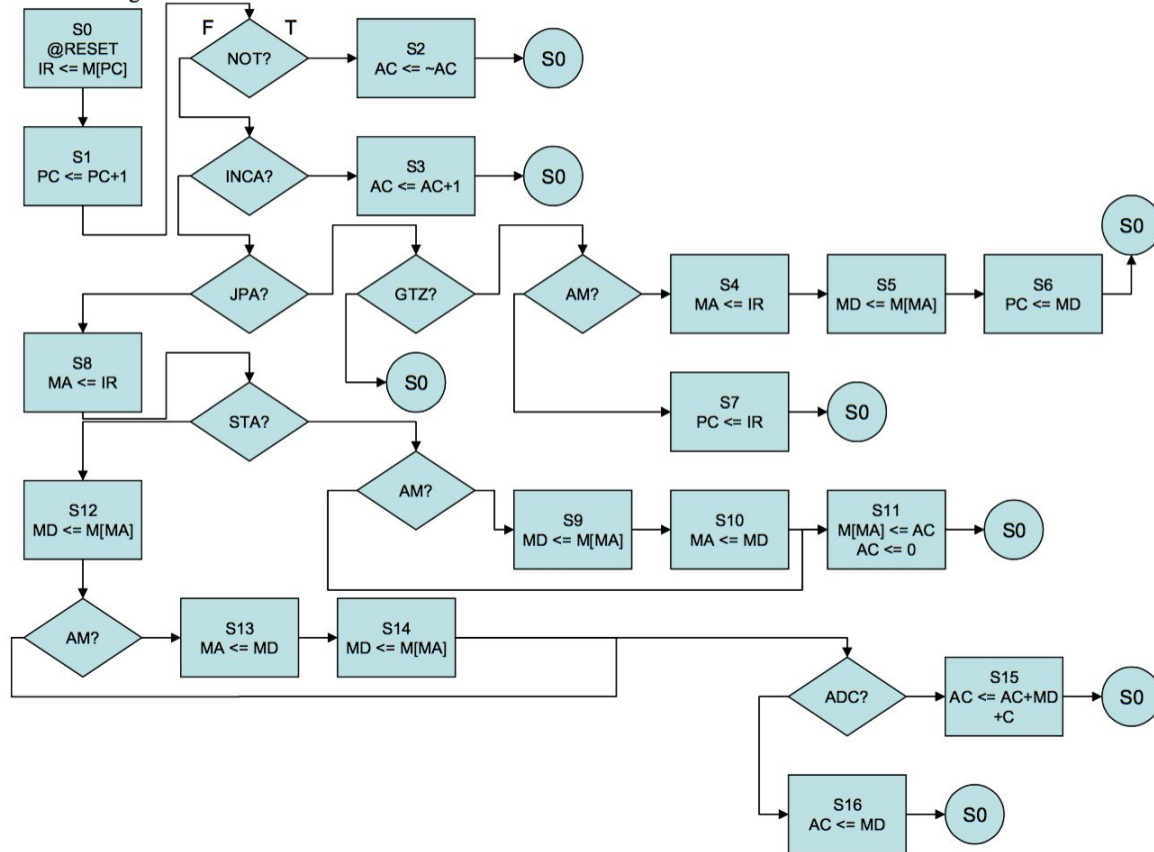

Architecture:

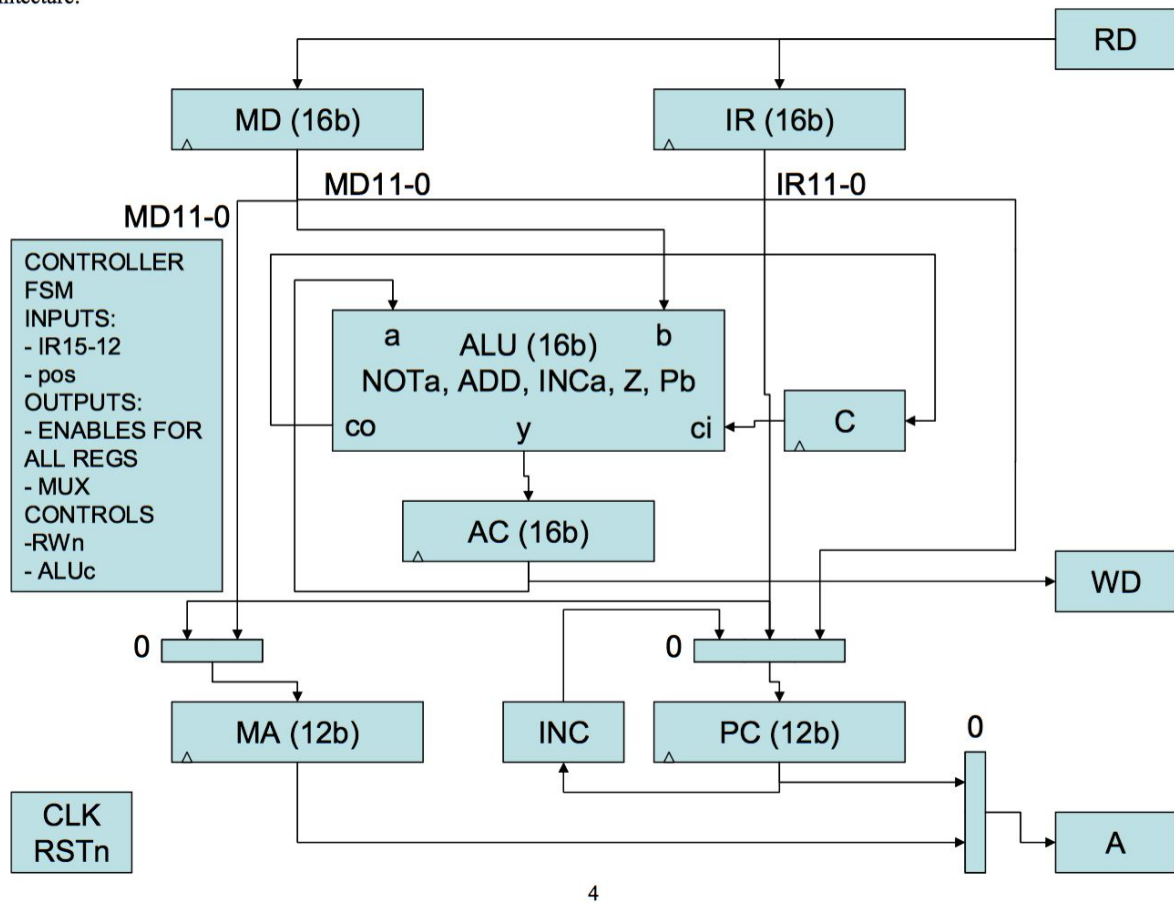

4

While utilizing the above constraints, students will implement the simple processor architecture.

Students must also provide waveform outputs for the architecture.

## Results:

Our team's results display the functionality of our simple processor implementation. We began the coding process by creating various modules to incorporate each component in the simple processor. All code from all modules are shown below.

### Alu module:

```
module alu(
input[15:0]a,b,
```

```

input[2:0] alu_control,
input ci,
output reg[15:0]y,
output reg co
    );
    always@(*)begin
case(alu_control)
000:y=~a; //not
001:{co,y}=a+b; //adc
011:y=a+1; //inca
100:y=0; //sta
101:y=b; //lda
endcase
end
endmodule

```

### **Controller Module:**

```

module controller(

input [3:0] opcode,
input clk,reset,
input[15:0] AC,
output reg enable_IR,enable_MD,enable_AC,enable_MA,enable_PC,mux1,mux3,RWn,
output [2:0] alu_control,
output reg[1:0] mux2,
reg[4:0] presentstate,nextstate
);
initial begin
presentstate=5'b00000;
end

always@(posedge clk) begin
presentstate=nextstate;
end
assign
alu_control= opcode[3:1];

always @ (presentstate) begin
    case(presentstate)
        5'b00000: begin //s0
            enable_IR=1;
            enable_MD=0;
            enable_AC=0;
            enable_MA=0;
            enable_PC=1;
            mux2=3;
            mux1=0;
            mux3=0;
            RWn=1;
            nextstate=5'b00001;

```

```

end

5'b00001: begin //s1
    enable_IR=0;
    enable_MD=0;
    enable_AC=0;
    enable_MA=0;
    enable_PC=1;
    mux2=0;
    mux1=0; //do not care
    mux3=0;
    RWn=0;
    if(opcode[3:1]==3'b000)begin
        nextstate=5'b00010; //s2
    end
    else if(opcode[3:1]==3'b011)begin
        nextstate=5'b00011;
    end
    else if(opcode[3:1]==3'b010)begin
        if(AC>0)begin
            if(opcode[0]==1)begin //AM is lsb of opcode
                nextstate=5'b00100; //s4
            end
            else
                nextstate=5'b00111;
            end
        end
        else
            nextstate=5'b00000;
        end
    end
    else
        nextstate=5'b01000;
    end

5'b00010:begin //s2
    enable_IR=0;
    enable_MD=0;
    enable_AC=1;
    enable_MA=0;
    enable_PC=0;
    mux2=0; // do not care
    mux1=0; //do not care
    mux3=0; //do not care
    RWn=0; //tells if writing out or reading in (used if reading from RD)
    nextstate=5'b00000;
end

5'b00011:begin //s3
    enable_IR=0;
    enable_MD=0;
    enable_AC=1;

```

```
enable_MA=0;
enable_PC=0;
mux2=0;// do not care
mux1=0;//do not care
mux3=0;//do not care
RWn=0;
nextstate=5'b00000;
end
```

```
5'b00100:begin //s4
enable_IR=1;
enable_MD=0;
enable_AC=0;
enable_MA=1;
enable_PC=0;
mux2=1;// do not care
mux1=0;//do not care
mux3=1;//do not care
RWn=0;
nextstate=5'b00101;
end
```

```
5'b00101:begin //s5 CONCERN
enable_IR=0;
enable_MD=1;
enable_AC=0;
enable_MA=1;
enable_PC=0;
mux2=2;
mux1=1;
mux3=1;
RWn=1; //Whenever state has M[something]
nextstate=5'b00110;
end
```

```
5'b00110:begin //s6
enable_IR=0;
enable_MD=1;
enable_AC=0;
enable_MA=0;
enable_PC=1;
mux2=3;          // MUXES?
mux1=1;
mux3=0;
RWn=0;
nextstate=5'b00000;
end
```

```
5'b00111:begin //s7
```



```

enable_IR=1;
enable_MD=0;
enable_AC=0;
enable_MA=0;
enable_PC=1;
mux2=1;
mux1=0;
mux3=0;
RWn=0;
nextstate=5'b00000;
end

5'b01000:begin //s8
enable_IR=1;
enable_MD=0;
enable_AC=0;
enable_MA=1;
enable_PC=0;
mux2=1;
mux1=0;
mux3=1;
RWn=0;
    if(opcode[3:1]==3'b100)begin
        if(opcode[0]==1)begin
            nextstate=5'b01001;
        end
        else
            nextstate=5'b01011;
        end
    else
        nextstate=5'b01100;
    end
end

5'b01001:begin // s9
enable_IR=0;
enable_MD=1;
enable_AC=0;
enable_MA=1;
enable_PC=0;
mux2=2;
mux1=1;
mux3=1;
RWn=1;
nextstate=5'b01010;
end

5'b01010:begin //s10
enable_IR=0;
enable_MD=1;
enable_AC=0;

```

```

enable_MA=1;
enable_PC=0;
mux2=2;
mux1=1;
mux3=1;
RWn=0;
nextstate=5'b01011;
end

```

```

5'b01011:begin //s11
enable_IR=0;
enable_MD=0;
enable_AC=1;
enable_MA=1;
enable_PC=0;
mux2=0;//do not care
mux1=0;//do not care
mux3=1;
RWn=1;
nextstate=5'b01010;
end

```

```

5'b01100:begin //s12
enable_IR=0;
enable_MD=1;
enable_AC=0;
enable_MA=1;
enable_PC=0;
mux2=2;
mux1=1;
mux3=1;
RWn=1;
if(opcode[0]==1)begin
    nextstate=5'b01101;
end
else begin
    if(opcode[3:1]==001)
        nextstate=5'b01111;
    else
        nextstate=5'b10000;
end
end

```

```

end

```

```

end

```

```

5'b01101:begin //s13
enable_IR=0;
enable_MD=1;
enable_AC=0;
enable_MA=1;
enable_PC=0;

```

```

        mux2=2;
        mux1=1;
        mux3=1;
        RWn=0;
nextstate=5'b01110;
    end

    5'b01110:begin //s14
        enable_IR=0;
        enable_MD=1;
        enable_AC=0;
        enable_MA=1;
        enable_PC=0;
        mux2=2;
        mux1=1;
        mux3=1;
        RWn=1;
        if(opcode[3:1]==001)
            nextstate=5'b01111;
        else
            nextstate=5'b10000;
        end
    end

```

```

    5'b01111:begin //s15
        enable_IR=0;
        enable_MD=1;
        enable_AC=1;
        enable_MA=0;
        enable_PC=0;
        mux2=2;
        mux1=1;
        mux3=0; //do not care
        RWn=0;
        nextstate=5'b00000;
    end

```

```

    5'b10000:begin //s16
        enable_IR=0;
        enable_MD=1;
        enable_AC=1;
        enable_MA=0;
        enable_PC=0;
        mux2=2;
        mux1=1;
        mux3=1;
        RWn=0;
    end

```

```

endcase

```

```
end
endmodule
```

**Data path module:**

```
module Datapath(
input mux1,mux3,enable_IR,enable_MD,enable_AC,enable_MA,enable_PC,RWn,clk,reset,
input[2:0]alu_control,
input[1:0]mux2,
input[15:0]RD,
output reg[11:0] A,
output reg [15:0] WD,AC, IR
);
reg[15:0] MD;
reg[11:0] MA,PC;
reg c ;//both ci and co
reg[15:0] alu_output;
```

```
initial begin
PC=0;
c=0;
A=0;
AC=0;
end
alu m1 (.a(AC),.b(MD),.y(alu_output),.ci(c),.co(c),.alu_control(alu_control));
```

```
always@(*)begin
if(enable_AC==1)
AC=alu_output;
```

```
end
```

```
always@(posedge clk)begin
case(RWn)
0:begin
if(enable_AC==1)
WD=AC;
end
1: begin
if(enable_IR==1)
IR=RD;
else if(enable_MD==1)
MD=RD;
end
endcase
//mux1
case(mux1)
```

```
0:begin
```

```

if(enable_MA == 1 && enable_IR==1)
    MA=IR;
end

1:begin
if(enable_MA == 1 && enable_MD==1)
    MA=MD;
end

endcase

case(mux2)

0:begin
if(enable_PC == 1)
    PC=PC+1;
end

1:begin
if(enable_PC == 1 && enable_IR==1)
    PC=IR;
end

2:begin
if(enable_PC == 1 && enable_MD==1)
    PC=MD;
end

endcase

case(mux3)

0:begin
if(enable_PC == 1)
    A=PC;
end

1:begin
if(enable_MA == 1)
    A=MA;
end

endcase
end
endmodule

```

### **CPU Module:**

```

module CPU(

```

```

input[15:0] RD,
input clk, reset,
output[15:0] WD,
output[11:0] A
);

```

```

wire mux1,mux3,enable_IR,enable_MD,enable_AC,enable_MA,enable_PC,RWn,clk,reset,RWn;
wire [1:0] mux2;
wire[15:0]AC;
wire[2:0]alu_control;
wire[15:0] IR;

```

Datapath m2

```

(.mux1(mux1),.mux2(mux2),.mux3(mux3),.enable_IR(enable_IR),.enable_MD(enable_MD),.enable_AC(enable_AC),.enable_MA(enable_MA),.enable_PC(enable_PC),.RWn(RWn),.alu_control(alu_control),clk(clk),.reset(reset),.RD(RD),.A(A),.WD(WD),.AC(AC),.IR(IR));

```

controller m3

```

(.opcode(IR[15:12]),.clk(clk),.reset(reset),.AC(AC),.enable_IR(enable_IR),.enable_MD(enable_MD),.enable_AC(enable_AC),.enable_MA(enable_MA),.enable_PC(enable_PC),.mux1(mux1),.mux2(mux2),.mux3(mux3),.RWn(RWn),.alu_control(alu_control));

```

Endmodule

### CPU testbench:

```

module CPU_test_hope;

```

```

    // Inputs

```

```

    reg [15:0] RD;

```

```

    reg clk;

```

```

    reg reset;

```

```

    // Outputs

```

```

    wire [11:0] A;

```

```

    wire [15:0] WD;

```

```

reg[15:0] instructionmem[63:0];

```

```

    // Instantiate the Unit Under Test (UUT)

```

```

    CPU uut (

```

```

        .RD(RD),

```

```

        .clk(clk),

```

```

        .reset(reset),

```

```

        .A(A),

```

```

        .WD(WD)

```

```

    );

```

```

    initial begin

```

```

        instructionmem[0]=16'b0000000000000001;//Not

```

```

        instructionmem[1]=16'b0010000000000010;//ADC

```

```

        instructionmem[2]=16'b0011000000000010;//ADC w AM=1

```

```

instructionmem[3]=16'b010000000000011;//JPA
instructionmem[4]=16'b010100000000011;//JPA w AM=1
instructionmem[5]=16'b011000000000100;//INCA
instructionmem[6]=16'b100000000000101;//STA
instructionmem[7]=16'b100100000000101;//STA w AM=1
instructionmem[8]=16'b101000000000111;//LDA
instructionmem[9]=16'b101100000000111;//LDA w AM=1

```

```

        RD = 0;
        clk = 0;
        reset = 1;

        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here

    end
    always @(clk) begin
        #1;
        clk <= ~clk;
    end

    always @(A) begin
        RD=instructionmem[A];

    end
    always@(WD)
    instructionmem[A]=WD;

endmodule

```

After utilizing the test bench to test our processor, our team captured the output waveform from the processor. The input is shown above in the Test Bench Module section of our code, and the waveform is shown below, in Figure 1.

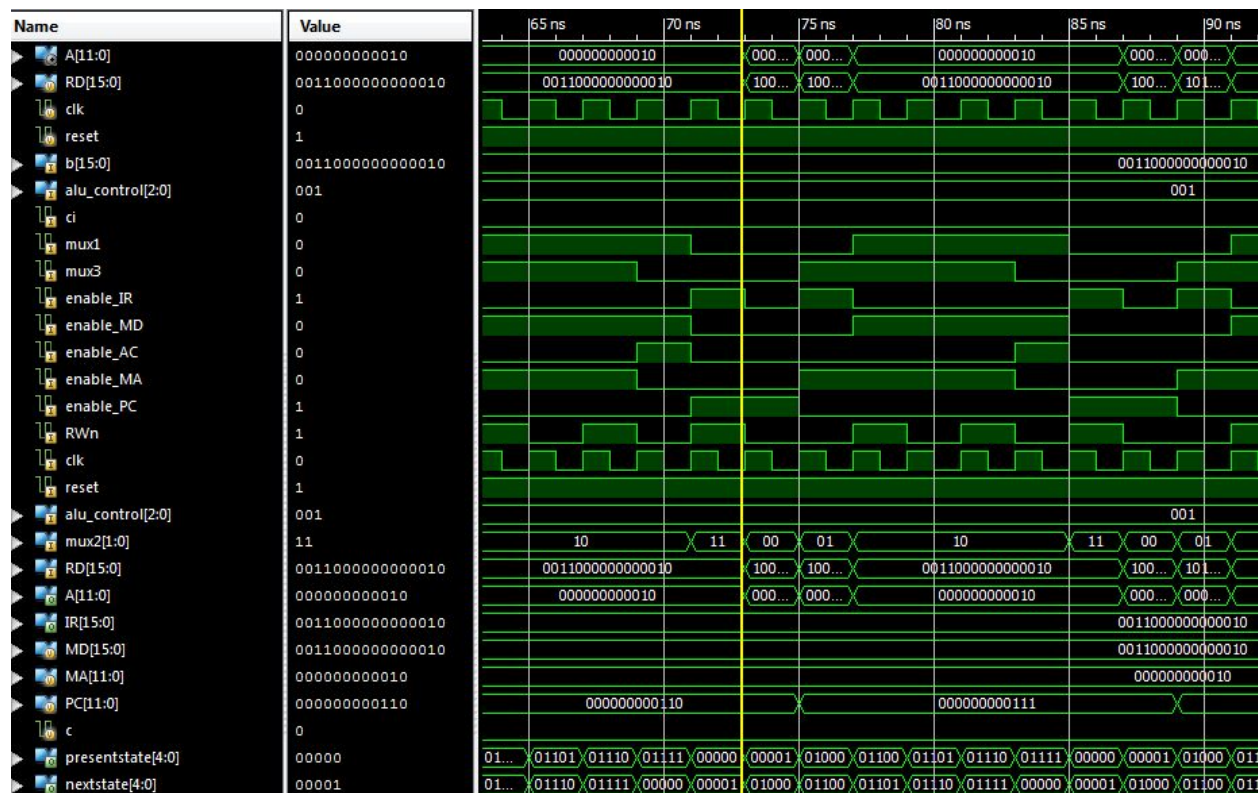


Figure 1: Waveform Output for Simple Processor

## Conclusions:

Overall, our team successfully implemented a simple processor architecture using Verilog. We implemented the proper code for each module, as well as initialized a testbench that takes machine code in as an input. We implemented the main components as modules, including an ALU module, a Controller module, a Data Path module, and a CPU module. The main takeaways from this lab are to understand the concept of a Von Neuman architecture, and understand the implementation of a simple processor in Verilog.