



XOR Gate Using CMOS Logic

Amauri Lopez and Bryan Guner

Dr. Pearlstein
ELC 383


XOR Gate Background

- Either A or B high will output high
- Both A and B high will output low
- Both A and B low will output low



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0


PSPICE CMOS Circuit Design

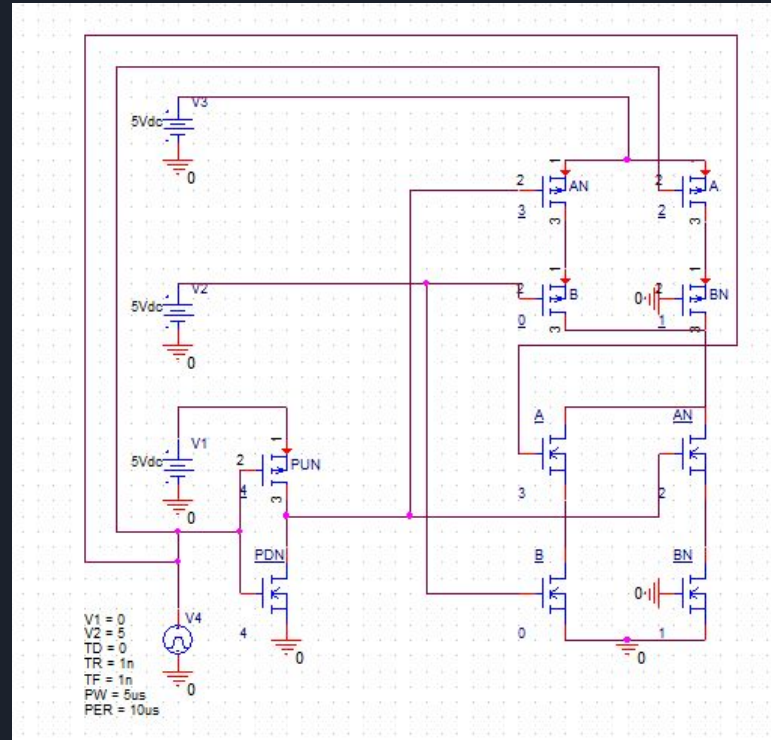


Simulation Results (Active Pull Up - Rising Edge)



 
Simulation Results (Active Pull Up - Falling Edge)



PSPICE RTL Circuit Design

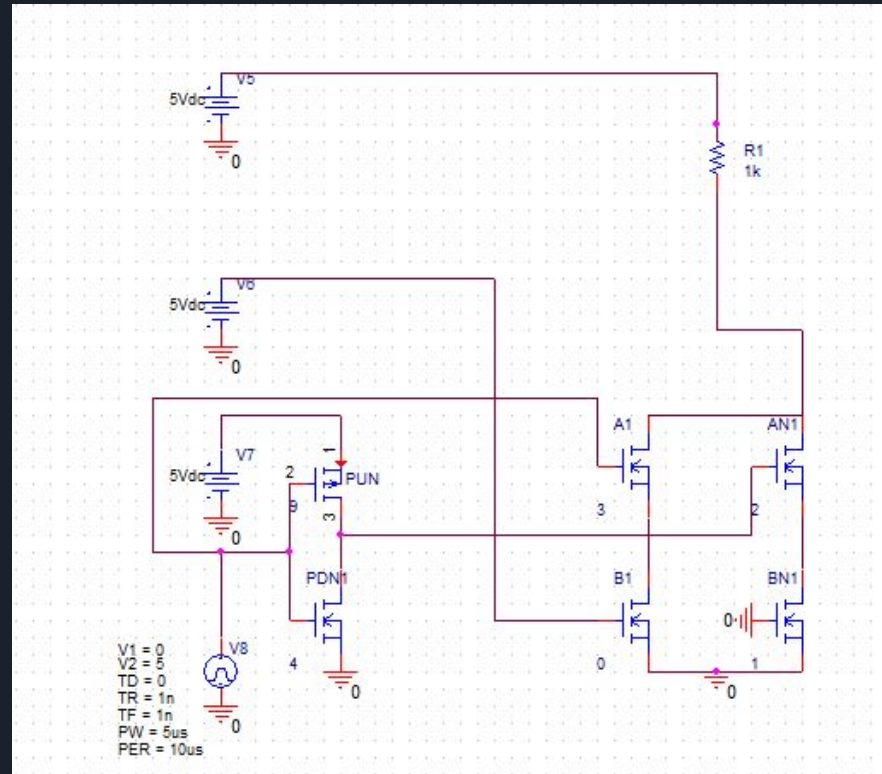

 
Simulation Results (Resistive pull up Rising edge 1k)




Simulation Results (Resistive pull up Falling edge 1k)



 
Simulation Results (Resistive pull up Rising edge 100k)



 Simulation Results (Resistive pull up Falling edge 100k)



Breadboard Design

 

Experimental Results (Falling Edge)



- Propagation delay between 50%-Input to 50%-Output approximately 50ns

Experimental Results (Rising Edge)



- Propagation delay between 50%-Input to 50%-Output approximately 50ns