

CMOS XOR Gate

Stephanie Fournier and Haley Scott



Theory of Operation

- When A is high, and B is low the output Y is high
- When both A and B are high, the output Y is 0
- An XOR gate differs from a simple OR gate, which would output high if both A and B were high

A	B	A'	B'	Y
0	0	1	1	0
1	0	0	1	1
0	1	1	0	1
1	1	0	0	0

Circuit Design Equations

$$\underline{Y = A \text{ XOR } B}$$

$$Y = AB' + A'B$$

Pull Up:

$$Y = AB' + A'B$$

Pull Down:

$$Y' = (AB' + A'B)'$$


$$Y' = (AB')' * (A'B)'$$

$$Y' = (A'+B) * (A+B')$$


$$Y' = (A*A') + (B*A') + (B*A) + (B*B')$$

$$Y' = (A*B) + (A'*B')$$

CMOS XOR Gate

 


Voltages Across the MOSFETS

 


X	Z
5 V	0 V

SPICE Simulations

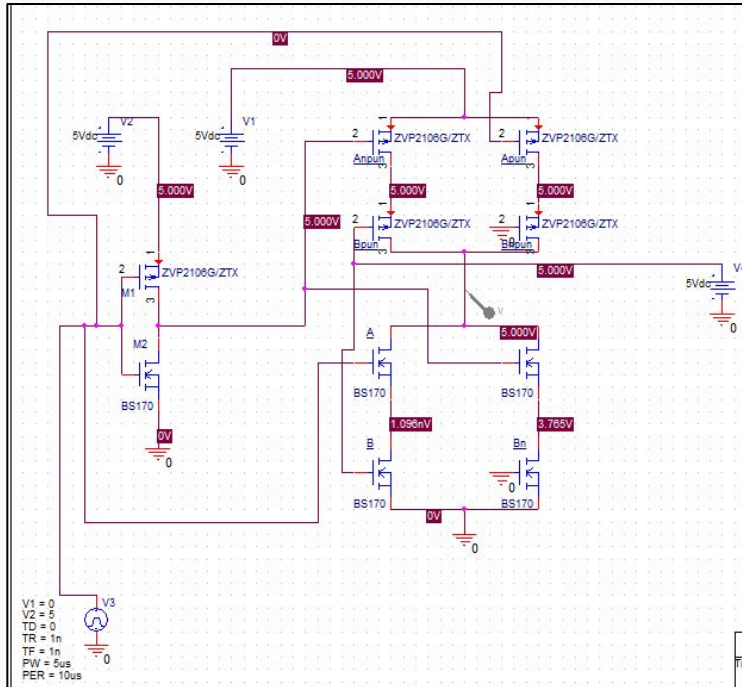

Active Pull-Up Network

Active Pull-Up Transient Time Response

 

Specifications::

- 5 us pulse width
- 10 us period time
- 100 us run time

Propagation time:

- 0.04 us




Specifications:

1. 50 us pulse width
2. 100 us period time
3. 1000 us run time

Propagation delay:


- 0.04 us

SPICE Simulations Continued

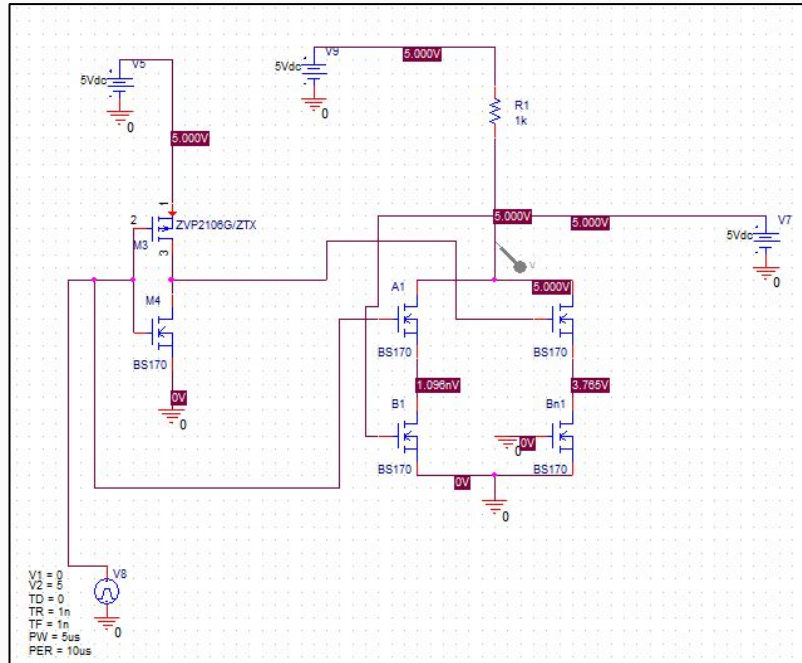

Resistive Pull-Up Network

Transient Time Response 1k Ohms

 


Specifications:

- 5 us pulse width
- 10 us period time
- 100 us run time

Propagation delay:

- 0.5 us

 


Specifications:

- 500 us pulse width
- 1000 us period time
- 10000 us run time


Propagation Delay:

- 0.55 us

Circuit Constructed

 

Results

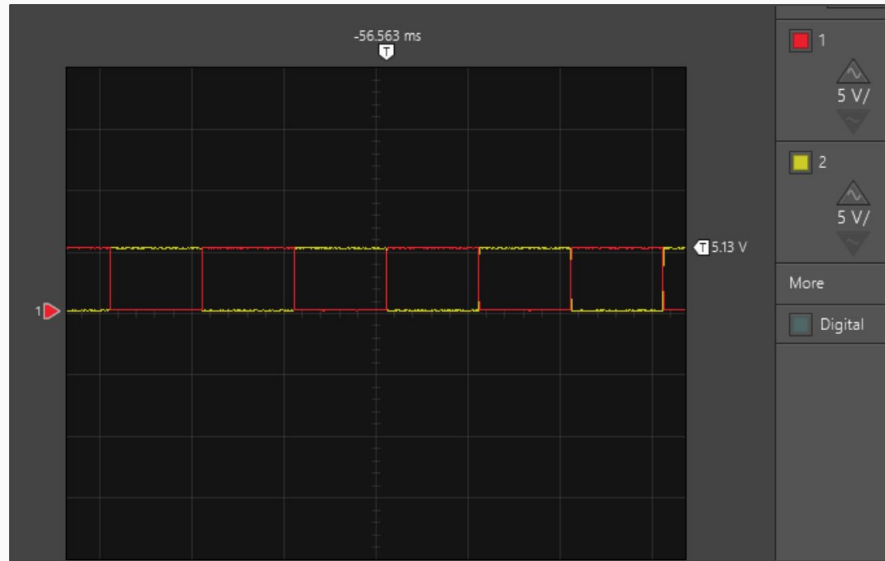

A	B	A'	B'	Y
0 V	0 V	5 V	5 V	.109 V
5 V	0 V	0 V	5 V	5.01 V
0 V	5 V	5 V	0 V	5.01 V
5 V	5 V	0 V	0 V	.109 V

Observations and Analysis

- Measured truth table aligns with theoretical truth table
- When voltage at the resistor is 0, the voltage = 5-0 so the power is $5^2/R$
- When voltage at the resistor is 5, the voltage = 5-5 so the power is 0